

▷ **16: Transients (B)**

**Piecewise steady
state inputs**

Sinusoidal Input

**Multiple
Discontinuities**

Switched Circuit

Transfer Function

**Transient from
Transfer Function**

Opamp Circuit

Transient

Summary

16: Transients (B)

Piecewise steady state inputs

16: Transients (B)

Piecewise steady

state inputs

Sinusoidal Input

Multiple

Discontinuities

Switched Circuit

Transfer Function

Transient from

Transfer Function

Opamp Circuit

Transient

Summary


We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:


$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.

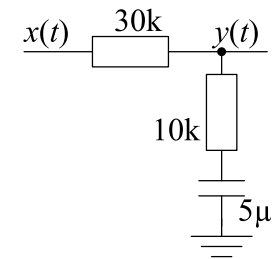Transient is always $y_{Tr}(t) = Ae^{-\frac{t}{\tau}}$ at each change.



[only one C or L]

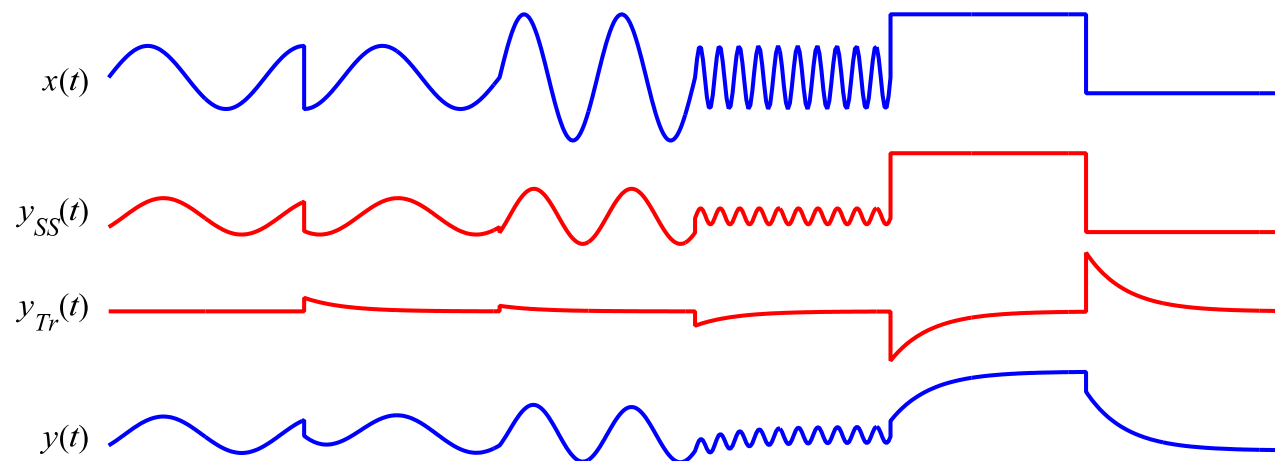

Sinusoidal Input

16: Transients (B)

Piecewise steady state inputs

▷ Sinusoidal Input

Multiple Discontinuities

Switched Circuit

Transfer Function

Transient from

Transfer Function

Opamp Circuit

Transient

Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$


Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$

$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198 \Rightarrow y_{Tr}(t) = 0.198e^{-t/\tau}$$

Complete Expression for $y(t)$
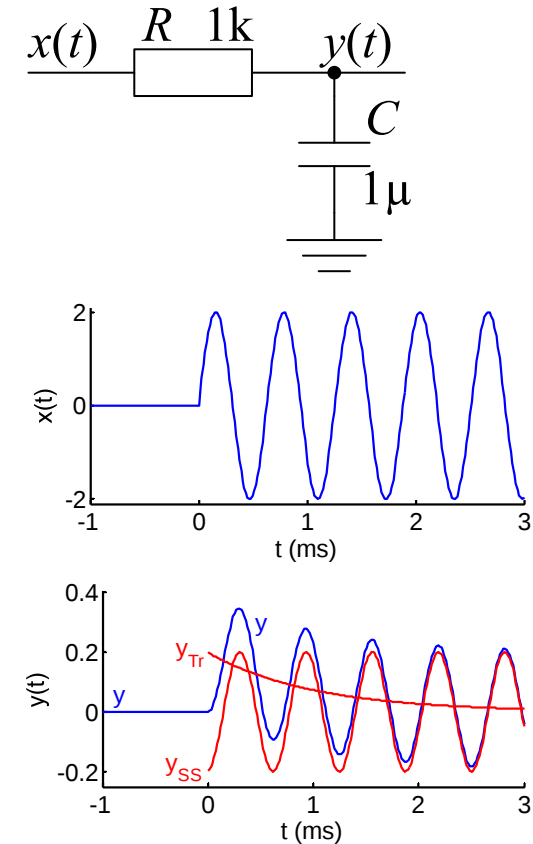
$$y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + Be^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)

$$y(0.00063+) = 0.59 \cos(0.00063\omega_2 - 169^\circ) + B$$




$$= 0.577 + B$$

$$y(0.00063-) = 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092$$

$$\Rightarrow 0.577 + B = -0.092 \Rightarrow B = -0.67 \Rightarrow y_{Tr} = -0.67e^{-(t-0.00063)/\tau}$$

Complete Expression for $y(t)$ (for $t \geq 0.63$ ms)
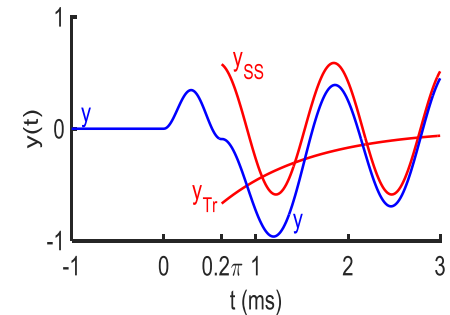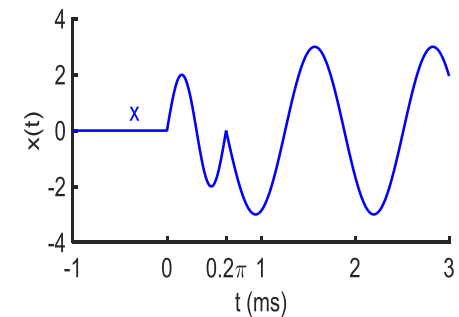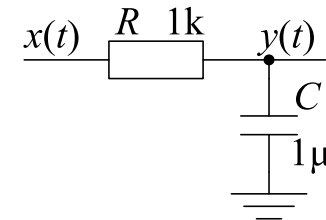
$$y(t) = 0.59 \cos(\omega_2 t - 169^\circ) - 0.67e^{-(t-0.00063)/\tau}$$



Switched Circuit

16: Transients (B)

Piecewise steady
state inputs

Sinusoidal Input

Multiple

Discontinuities

▷ Switched Circuit

Transfer Function

Transient from

Transfer Function

Opamp Circuit

Transient

Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

$$y(2-) = 9 - 9e^{-2/0.9} = 8.02$$




Switch opened at $t = 2$.

$$y_{SS} = 0\text{ V}$$

$$y(t) = 0 + Ae^{-(t-2)/\tau_O}$$

$$y(2+) = A = y(2-) = 8.02$$

$$y(20) = 8.02e^{-(20-2)/9} = 1.09$$

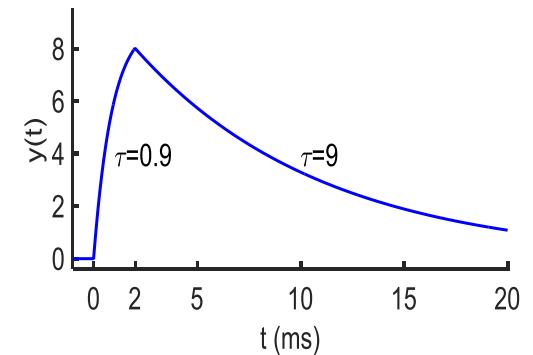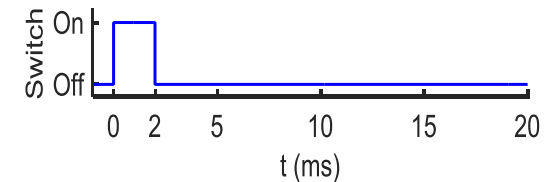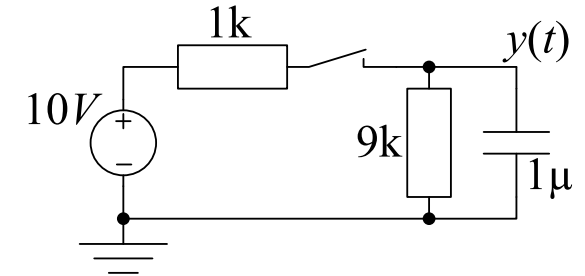

Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$

Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$




Denominator is always $(j\omega\tau + 1)$

Linearity: $Y = aX + bV$

$$\text{KCL @ supernode: } \frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$

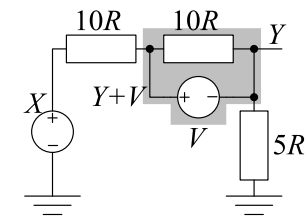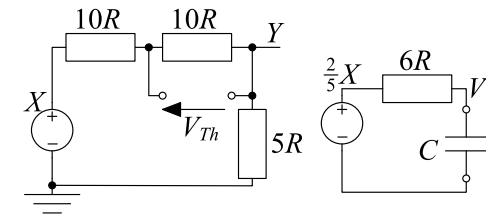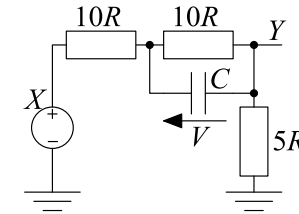Denominator of bV is unchanged by adding aX



(1) Denominator corner frequency is always $\frac{1}{\tau}$ for any transfer function in the circuit.

(2) $V = 0$ at $\omega = \infty$, so since $Y = aX + bV$, $a = \frac{Y}{X} \Big|_{\omega=\infty}$ (= HF-gain)

V is never discontinuous so ΔY discontinuity = HF-gain $\times$ ΔX discontinuity

Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$




Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$

$$(3\frac{1}{4} + A) - (-3\frac{1}{4}) = 2 \Rightarrow A = -4\frac{1}{2}$$

Complete Expression
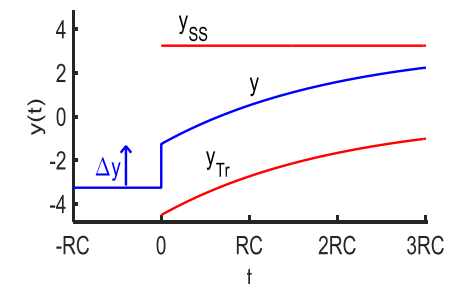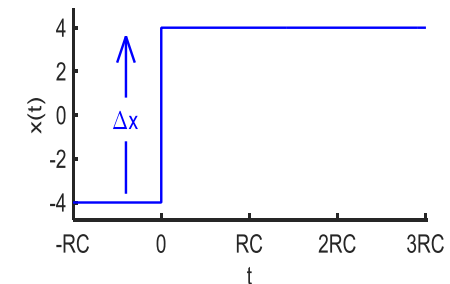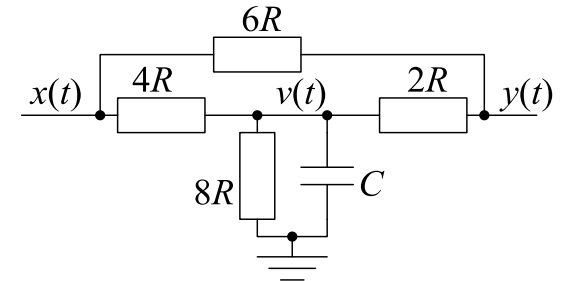
$$t \geq 0: y(t) = 3\frac{1}{4} - 4\frac{1}{2}e^{-t/2RC}$$



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$




Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$

$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$

Complete Expression

$$t \geq 0: y(t) = -4 + 2e^{-t/8RC}$$

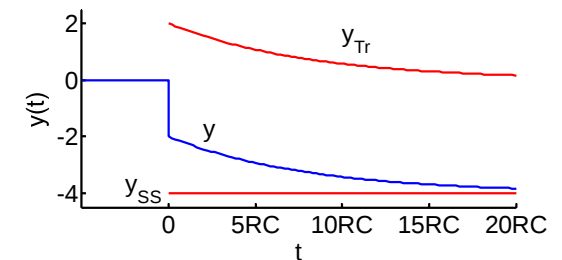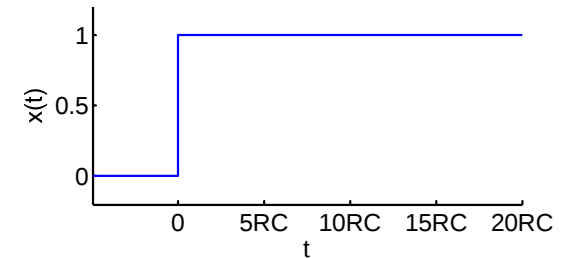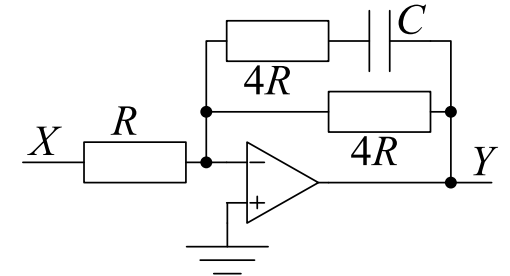

For opamp circuits get τ from the transfer function because R_{Th} is difficult to work out.

Summary

16: Transients (B)

Piecewise steady
state inputs

Sinusoidal Input

Multiple
Discontinuities

Switched Circuit

Transfer Function

Transient from
Transfer Function

Opamp Circuit
Transient

▷ Summary

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis $\rightarrow$ transfer function
- **Transient:** $Ae^{-t/\tau}$ where:
 - Two methods to find τ :
 - ▷ **Thévenin seen by L or C :** $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - ▷ **Transfer function denominator:** $(aj\omega + b) \Rightarrow \tau = \frac{1}{\omega_c} = \frac{a}{b}$
 - Two methods to find A :
 - ▷ **Continuity:** $\Delta V_C = 0$ or $\Delta I_L = 0$
 - ▷ **Discontinuity gain:** $\Delta \text{output} = \text{HF gain} \times \Delta \text{input}$

For further details see Hayt Ch 8 or Irwin Ch 7.