

Lecture 6


Active Filters

Prof Peter YK Cheung
Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk

Transfer Function of 1st order LP Filter

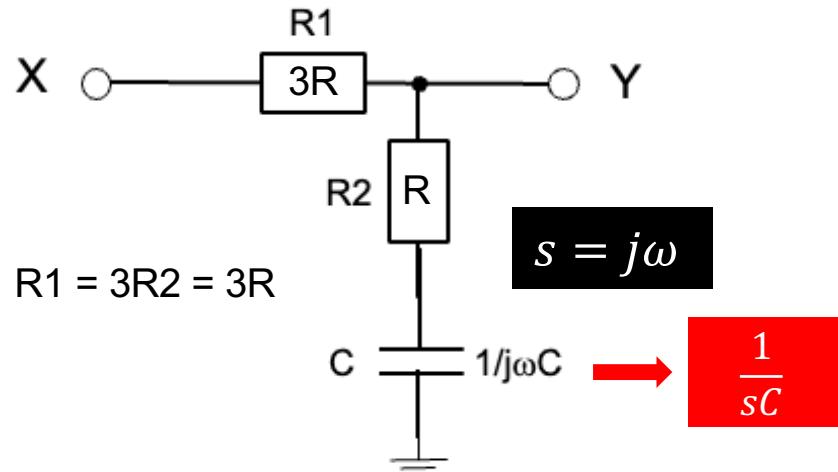From Year 1 ADC Part 1 Lecture 11, slide 3.



- ❖ More general if use **complex frequency s** to represent the quantity $j\omega$.
- ❖ Covered in Signals and Systems module this term, and Control Systems next term.
- ❖ Express impedance of capacitor as $\frac{1}{sC}$ instead of $\frac{1}{j\omega C}$.
- ❖ Capture both steady state (ac) and transient behaviour .


- ❖ Transfer function defined as:

$$H(s) = \frac{Y(s)}{X(s)} = \frac{R+1/sC}{4R+1/sC} = \frac{1+sRC}{1+4sRC}$$

- ❖ Frequency response is calculated as


$$H(s)|_{s=j\omega} = \frac{Y(j\omega)}{X(j\omega)} = \frac{1+j\omega RC}{1+4j\omega RC}$$

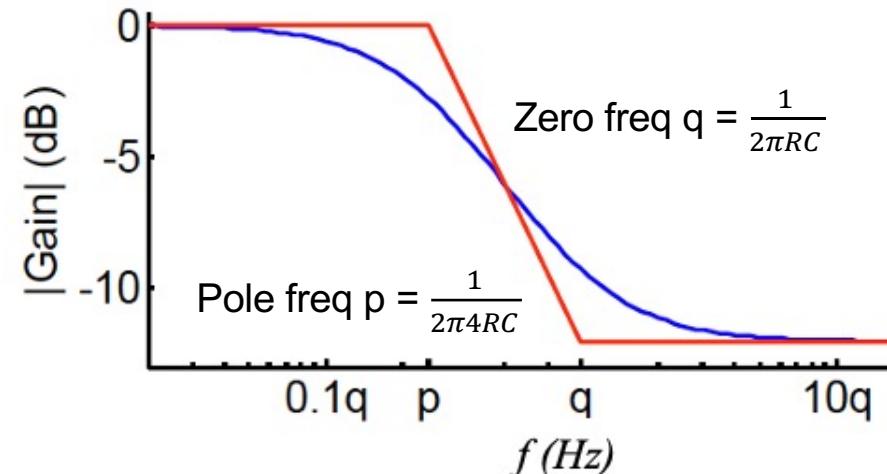- ❖ Easier to perform algebra manipulation than using $j\omega$.
- ❖ Provides better intuitions on system behaviour.
- ❖ This simple filter is first-order low-pass with 1 pole and 1 zero.
- ❖ The break frequency occurs when real and imaginary parts are equal in numerator (zero freq) and denominator (pole freq).




1st order Active Filter


1st order passive filter
with 1 pole

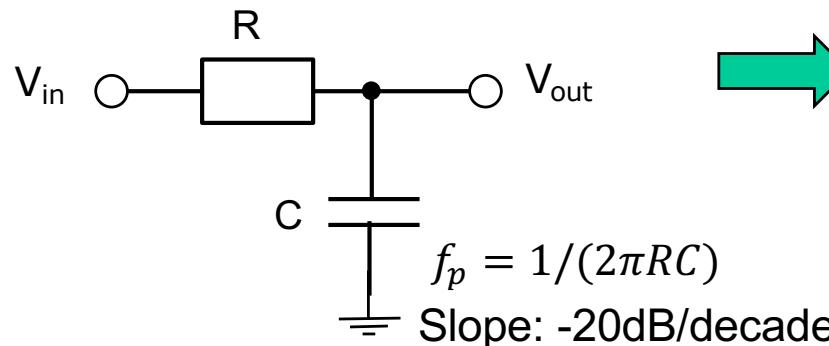

1st order active filter
gain of 1

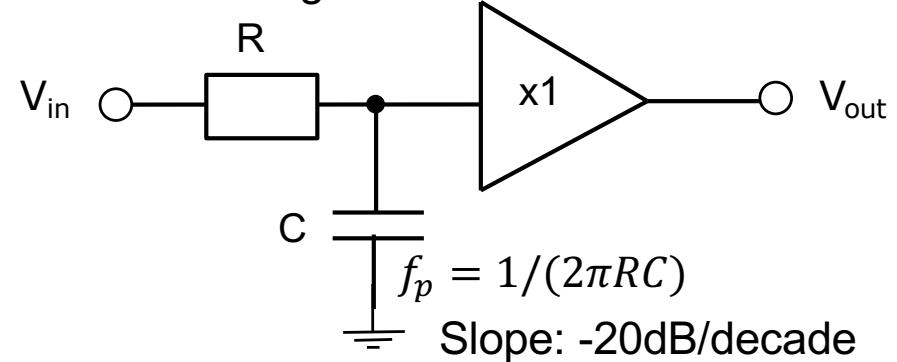


1st order active filter
gain of K

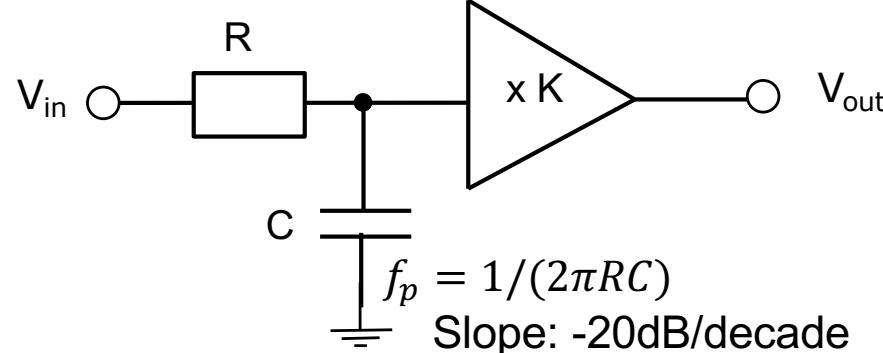

$$H(s)|_{s=j\omega} = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{K}{1+j\omega RC}$$


2nd order Active Lowpass Filter

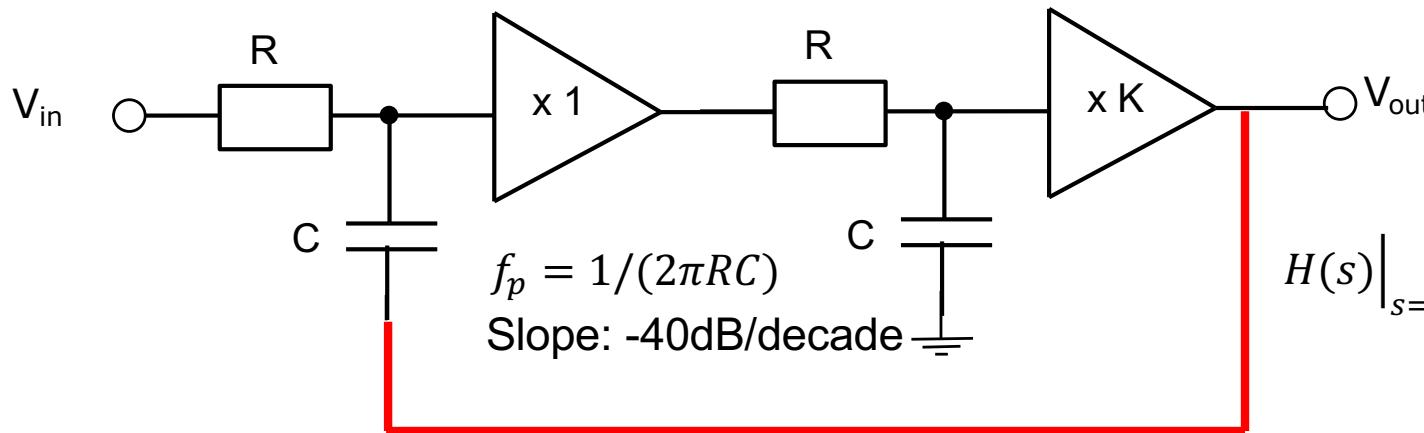2nd order active filter with
2 poles and dc gain of K



$$H(s)|_{s=j\omega} = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{K}{(1 + j\omega RC)^2}$$


2nd order Sallen-Key Filter (1955)

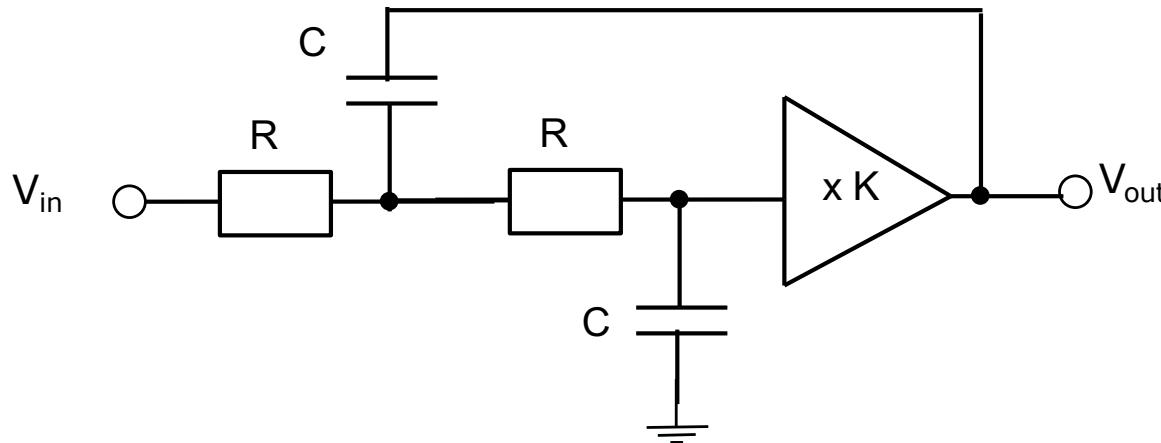

$$f_p = 1/(2\pi RC)$$

DC gain: K
Slope: -40dB/decade

Sallen-Key Filter Topology

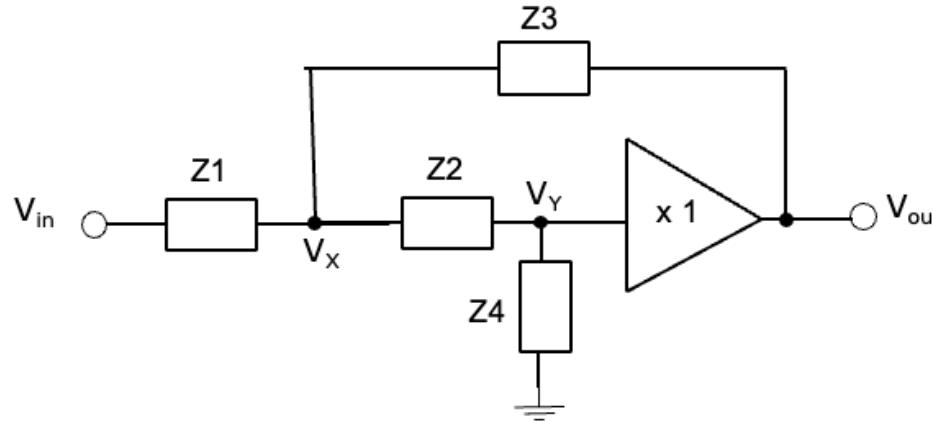

- ❖ Invented by R.P. Sallen and E.L. Key in 1955 using valves as active devices (!)
- ❖ Z_1 to Z_4 are arbitrary impedance from resistors, capacitors or inductors.
- ❖ Assume amplifier gain is 1 (can be generalised to K), $V_Y = V_{out}$.
- ❖ Apply KCL to V_x yields:

$$\frac{V_{in} - V_x}{Z_1} + \frac{V_{out} - V_x}{Z_3} + \frac{V_{out} - V_x}{Z_4} = 0$$


- ❖ Apply KCL at V_Y yields:

$$V_x = V_{out} + \frac{Z_2}{Z_4}V_{out} = V_{out}(1 + \frac{Z_2}{Z_4})$$

- ❖ Combining the two gives a general transfer function equation:

$$\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

2nd order Sallen-Key Lowpass Filter

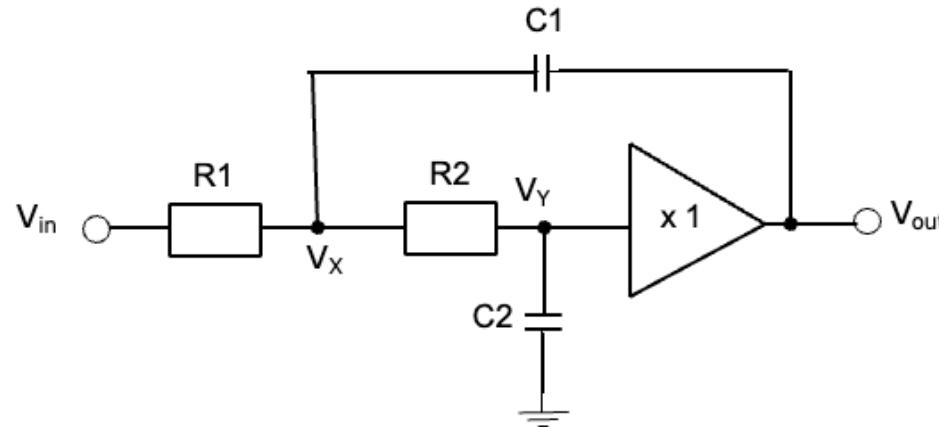

$$\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

$$Z_1 = R_1, \quad Z_2 = R_2$$

$$Z_3 = 1/sC_1, \quad Z_4 = 1/sC_2$$


- ❖ Using the transfer function equation $H(s)$ from previous slice:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{s^2 C_1 C_2}}{R_1 R_2 + \frac{1}{sC_1} (R_1 + R_2) + \frac{1}{s^2 C_1 C_2}}$$

- ❖ Rearrange and put this in a standard form for a 2nd order lowpass system:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \textcolor{red}{C_2(R_1 + R_2)} s + \textcolor{green}{C_1 C_2 R_1 R_2} s^2}$$

Significance of ω_0 and Q (1)

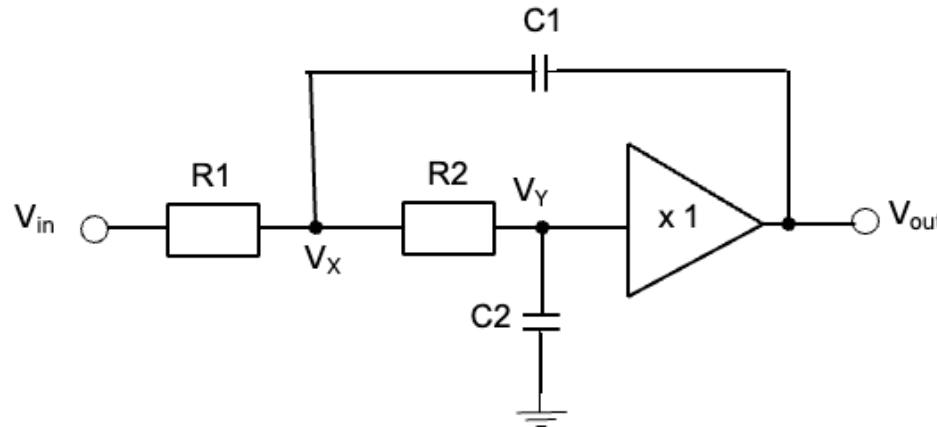

$$Z_1 = R_1, \quad Z_2 = R_2$$

$$Z_3 = 1/sC_1, \quad Z_4 = 1/sC_2$$

- Put this into the standard form of a 2nd order lowpass filter is:

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{\omega_0 Q} s + \frac{1}{\omega_0^2} s^2} = \frac{1}{1 + \textcolor{red}{C_2(R_1+R_2)} s + \textcolor{green}{C_1 C_2 R_1 R_2} s^2}$$

Q is the quality factor
 ζ is the damping ratio
 $Q = \frac{1}{2\zeta}$

$$\frac{2\zeta}{\omega_0} = \frac{1}{\omega_0 Q}$$

$$\frac{1}{\omega_0^2}$$

ω_0 is the cutoff frequency (rad/s)


$$f_c = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{C_1 C_2 R_1 R_2}} \text{ in Hz}$$

- Therefore, the cutoff frequency is: $f_c = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{C_1 C_2 R_1 R_2}}$ Hz
- The quality factor Q is: $Q = \frac{\sqrt{C_1 C_2 R_1 R_2}}{C_2(R_1+R_2)}$

Significance of ω_0 and Q (2)


- ❖ Rewrite the transfer function as:
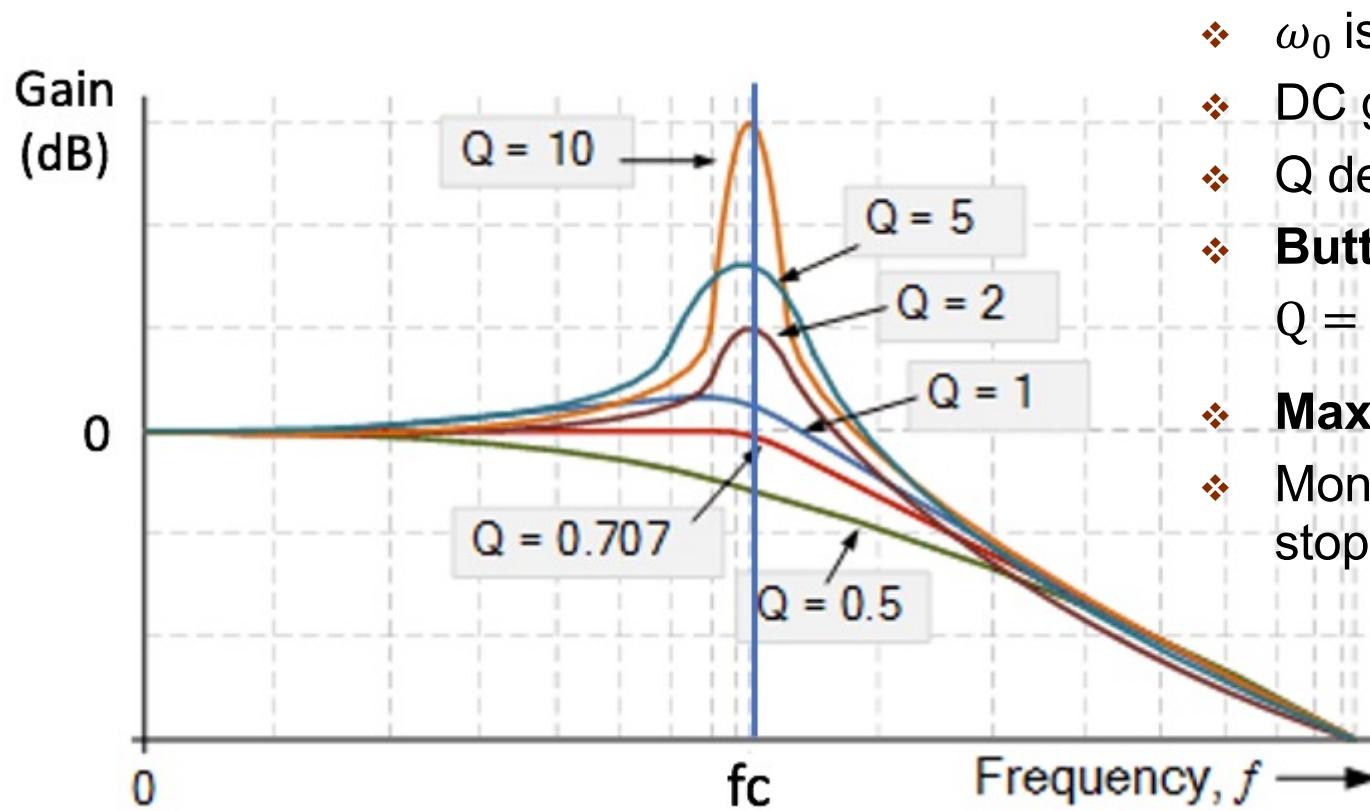
$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \frac{1}{\omega_0 Q} s + \frac{1}{\omega_0^2} s^2} = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \quad f_0 = \frac{\omega_0}{2\pi}$$





- ❖ ω_0 is the **cut-off frequency** of filter.
- ❖ DC gain of filter is 1 (i.e. $s=0$).
- ❖ Q determine how 'peaky' the filter is.
- ❖ **Butterworth filter:** $2\zeta = 1.414$, $Q = \frac{1}{2\zeta} = 0.707$.
- ❖ **Maximally flat** gain in passband
- ❖ Monotonically decreasing gain in stop band.

A simple Sallen-Key filter (from Lab 2)

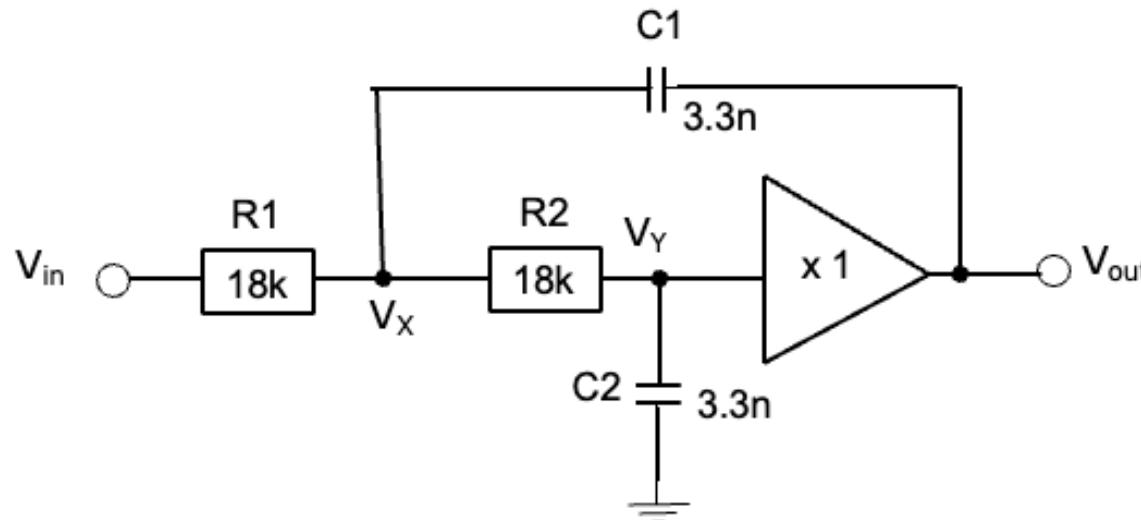

- ❖ Simplify by making $R_1 = R_2 = R = 18k\Omega$, and $C_1 = C_2 = C = 3.3nF$.
- ❖ The cutoff frequency is: $f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{2\pi R C} = 2.7\text{kHz}$ and
- ❖ $Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_2(R_1 + R_2)} = \frac{RC}{(C \times 2R)} = \frac{1}{2}$.
- ❖ This is NOT a Butterworth filter because Q is not 0.707 or $\frac{1}{\sqrt{2}}$.

Sallen-Key filter with gain = K

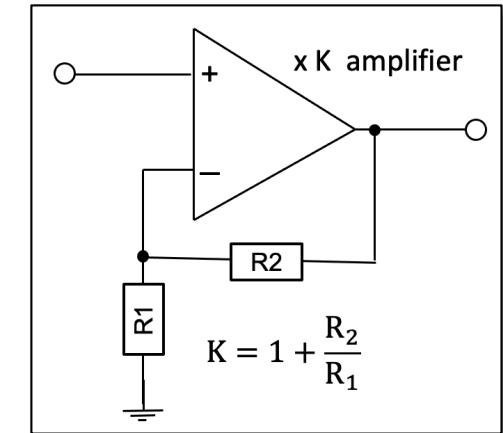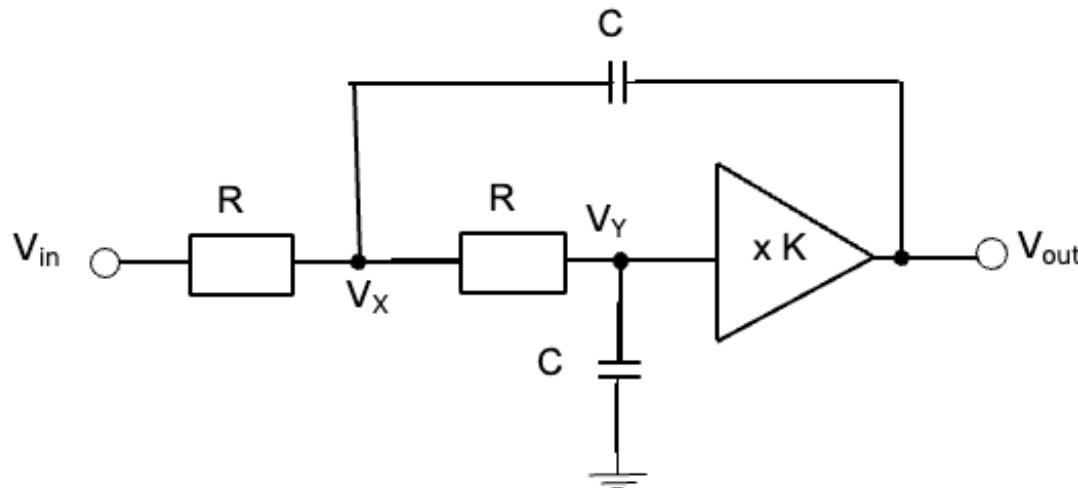


- ❖ Keep same R and C values, fix Q by changing gain of op-amp K
- ❖ Left as an exercise to proof:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = K \times \frac{1}{1 + (3 - K)RC s + R^2 C^2 s^2}$$

- ❖ Therefore, cutoff frequency f_c is same as before: $f_c = \frac{1}{2\pi\omega_0} = \frac{1}{2\pi RC}$.
- ❖ And, $Q = \frac{1}{\omega_0} \times \frac{1}{(3-K)RC} = \frac{1}{3-K}$.
- ❖ Therefore, to get a Butterworth filter with this topology, $Q = 0.707$, and
- ❖ $K = 3 - \frac{1}{Q} = 1.586$.




General Procedure: Butterworth LP filter

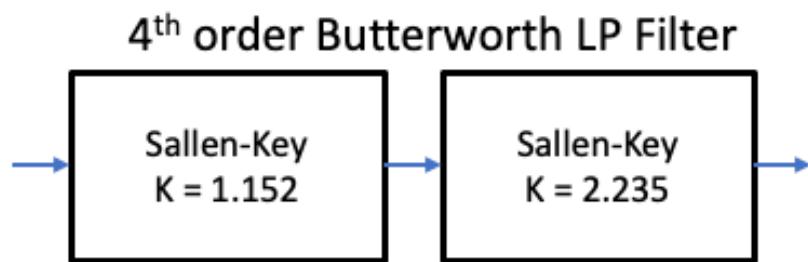1. Determine the required cutoff frequency f_c .
2. Calculate R and C product with: $RC = \frac{1}{2\pi f_c}$.
3. Pick a suitable value of C \gg input capacitance of op-amp (say in nF range).
4. Calculate value of R to give the required cutoff frequency.
5. Determine order of filter depending on required attenuation rate. Filter attenuation rate is $-20 \times n$ dB/decade, for an nth order filter.
6. Round n to the nearest high even number. You will need $n/2$ Sallen-Key filter stages.
7. Use the table below to design gain of each stage of the filter. For example, for a 4th order Butterworth filter, we need two Sallen-Key stages with gain of 1.152 followed by 2.235.
8. Choose resistors for op-amps feedback paths to provides specified gain values.



ORDER n	Gain values K
2	1.586
4	1.152, 2.235
6	1.068, 1.586, 2.483
8	1.038, 1.337, 1.889, 2.610

Other Sallen-Key filter circuits

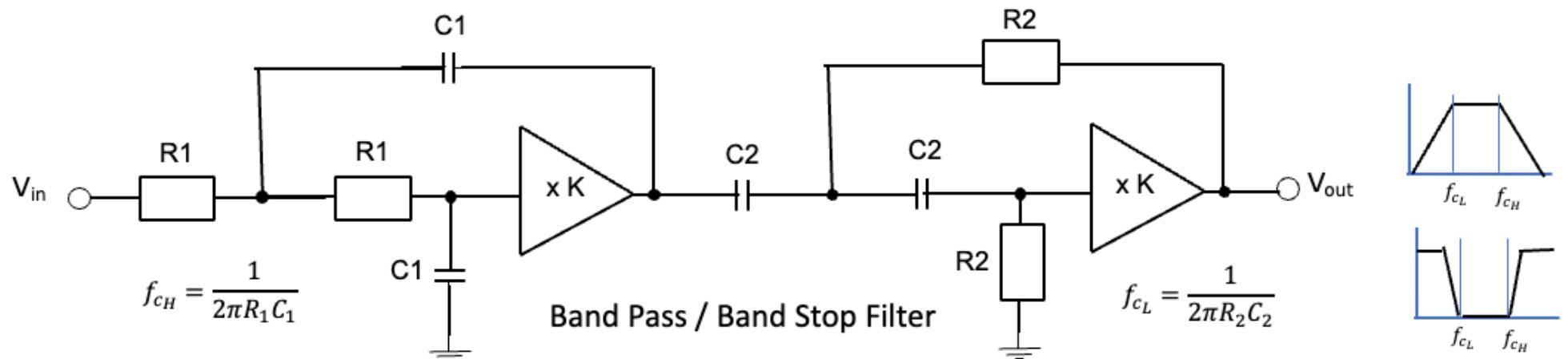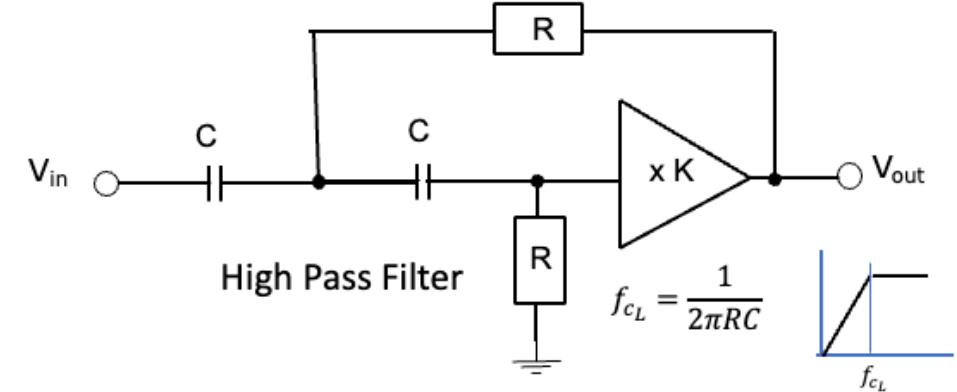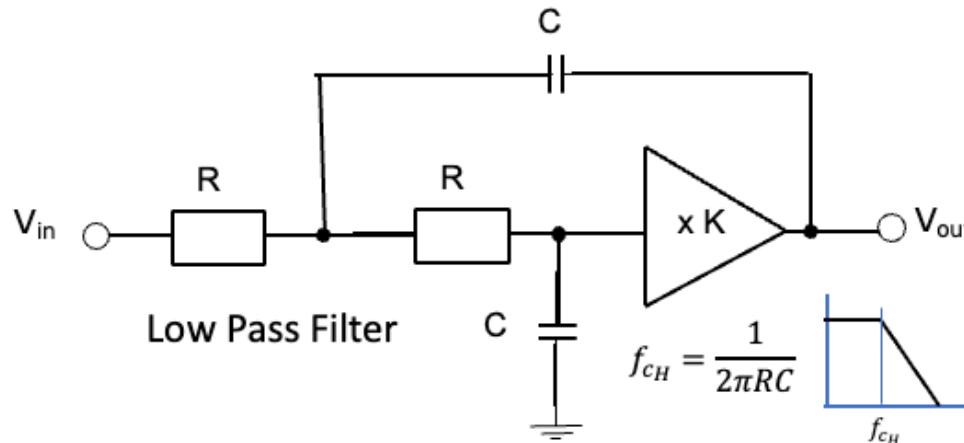


Using different values for R1 and R2

- ❖ Revisit transfer function of filter from slide 7::

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{\omega_0 Q} s + \frac{1}{\omega_0^2} s^2} = \frac{1}{1 + C(R_1 + R_2) s + C^2 R_1 R_2 s^2}$$

$$Q = \frac{\sqrt{R_1 R_2}}{R_1 + R_2}$$
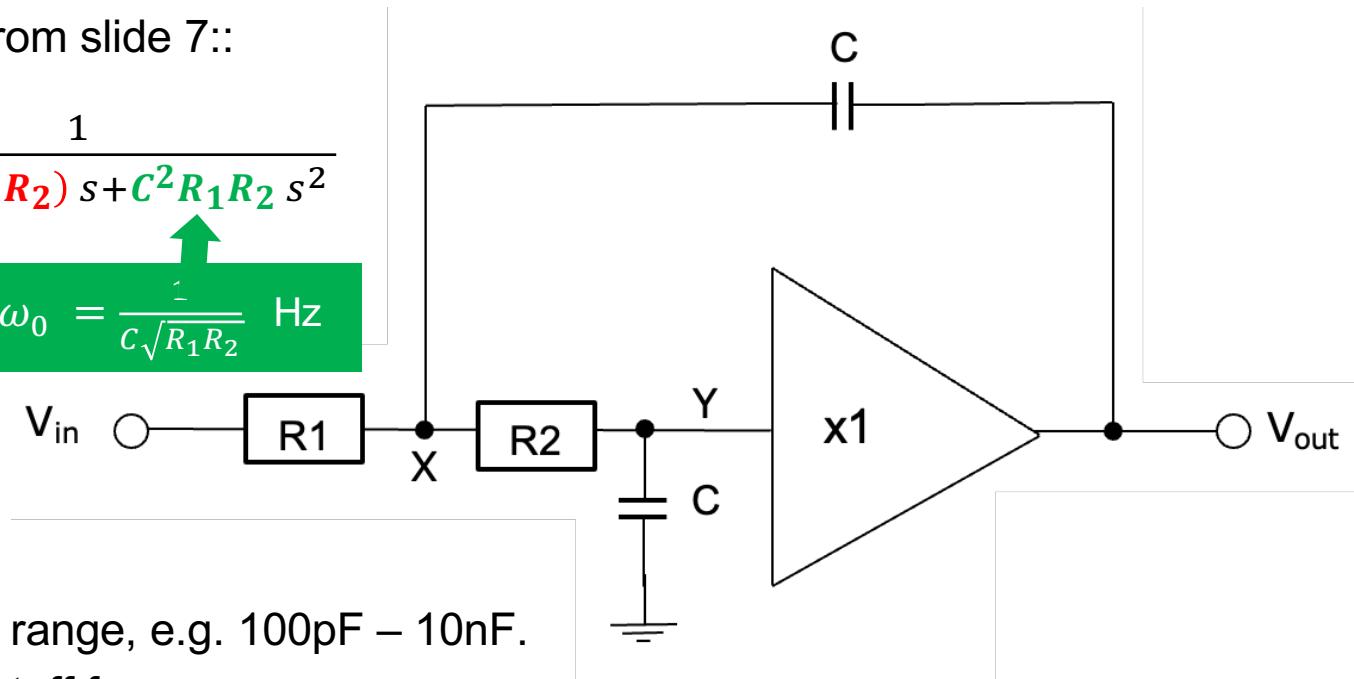
$$\omega_0 = \frac{1}{C \sqrt{R_1 R_2}} \text{ Hz}$$



- ❖ Design step:
 - Choose C in a reasonable range, e.g. 100pF – 10nF.
 - ❖ Write down eq.1 for a given cutoff frequency.
 - ❖ Write down eq. 2 for a given Q value.
 - ❖ Solve the two equations for R1 and R2 values.