

## Topic 11 Pass Transistor Logic

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London

Reading: "Top-Down Pass-Transistor Logic Design", K. Yano etc., IEEE J. of Solid-State Circuits, Vol 31, No. 6, June 1996.

URL: [www.ee.ic.ac.uk/pcheung/](http://www.ee.ic.ac.uk/pcheung/)  
E-mail: [p.cheung@ic.ac.uk](mailto:p.cheung@ic.ac.uk)


### Complementary Pass-transistor Logic (CPL)

- ◆ "A 3.8 ns CMOS 16 x 16b Multiplier Using Complementary Pass-Transistor Logic" by K. Yano etc., IEEE J. of Solid-state Circuits, Vol 15, No 2, April 1990.
- Logic network employs input signals at both gate and drain terminals.
- Inputs and Outputs are always complementary.
- Outputs from network provide strong '0's but weak '1's. Inverters and PMOS pull-ups provide amplification and buffering as necessary.

## Recent development in PTL

- New development by designers at Hitachi Japan in the last 10 years.
- Three circuit styles proposed:
  - Complementary Pass-transistor Logic (CPL), 1990
  - Double Pass-transistor Logic (DPL), 1993
  - Lean Integration with Pass-transistors (LEAP), 1996
- All exploit pass-transistors to implement general logic functions
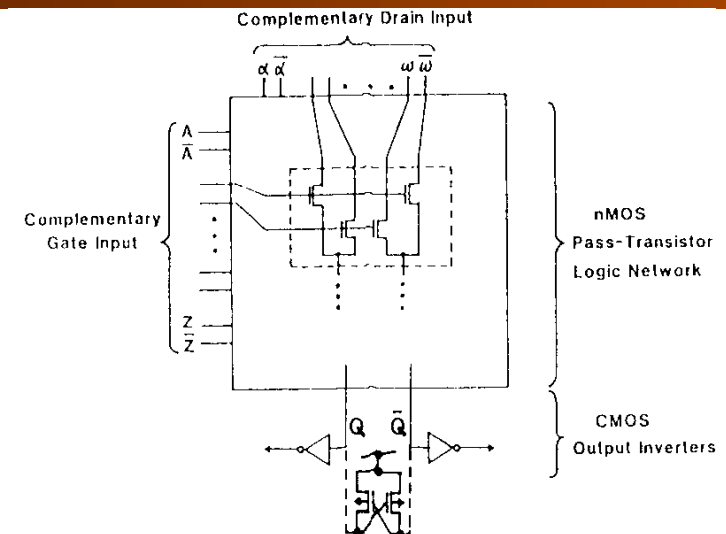
### Complementary Pass-transistor Logic (CPL)



## Basic gates designed in CPL

Circuit				
Logic Function				

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 5

## 3-input gates designed in CPL

Circuit			
Logic Function			

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 6

## CPL based 1-bit full adder


	CMOS	CPL
Full Adder Circuit		
Transistor Count	40	28
Area	4730 $\mu\text{m}^2$	4218 $\mu\text{m}^2$
Delay (4V)	0.63ns	0.26ns
Power (100MHz)	1.2mW	0.86mW

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 7

## Advantages of CPL

 

Nov-23-09

E4.20 Digital IC Design


Topic 11 - 8

## Double Pass-transistor Logic (DPL)

- “A 1.5-ns 32-b CMOS ALU in Double Pass-Transistor Logic”, M. Suzuki etc., IEEE J. of Solid-State Circuits, Vol 28, No 11, Nov., 1993

	CPL	CMOS	DPL																																																												
Circuit																																																															
Truth Table & Operation	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td><math>\bar{B}</math></td></tr> <tr><td>1</td><td>1</td><td>0</td><td><math>\bar{B}</math></td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1		1	0	1	$\bar{B}$	1	1	0	$\bar{B}$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td><math>\bar{B}</math></td></tr> <tr><td>1</td><td>1</td><td>0</td><td><math>\bar{B}</math></td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1		1	0	1	$\bar{B}$	1	1	0	$\bar{B}$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td><math>\bar{A}</math></td></tr> <tr><td>0</td><td>1</td><td>1</td><td><math>\bar{A}</math></td></tr> <tr><td>1</td><td>0</td><td>1</td><td><math>\bar{B}</math></td></tr> <tr><td>1</td><td>1</td><td>0</td><td><math>\bar{A}</math></td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	$\bar{A}$	0	1	1	$\bar{A}$	1	0	1	$\bar{B}$	1	1	0	$\bar{A}$
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1																																																													
1	0	1	$\bar{B}$																																																												
1	1	0	$\bar{B}$																																																												
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1																																																													
1	0	1	$\bar{B}$																																																												
1	1	0	$\bar{B}$																																																												
A	B	XOR	Pass																																																												
0	0	0	$\bar{A}$																																																												
0	1	1	$\bar{A}$																																																												
1	0	1	$\bar{B}$																																																												
1	1	0	$\bar{A}$																																																												
Swing	$0 \leftrightarrow (V_{cc} - V_{th})$	$0 \leftrightarrow V_{cc}$	$0 \leftrightarrow V_{cc}$																																																												

## Basic gates in DPL

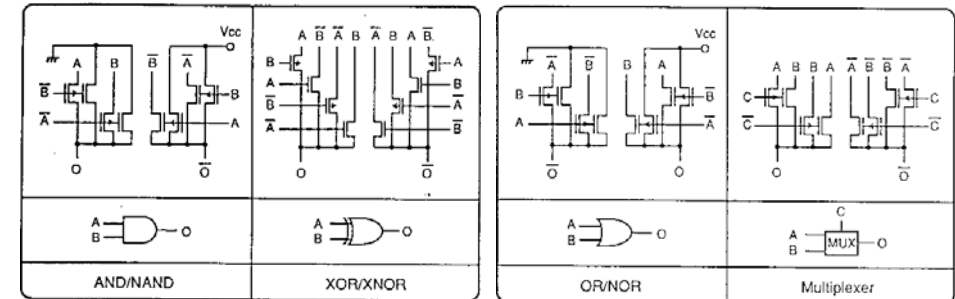


## Why is DPL faster?


	CPL	CMOS	DPL
Current Path			
Equiv. Circuit			
Equiv. Resistance	$\frac{4}{3}R$	$\frac{3}{2}R$	$R$
 
## Sum circuit in DPL


- This adder circuit is extremely elegant. We have shown that for 0.6 micron technology, it offers up to 20% faster operating speed when compare with normal CMOS with only marginal increase in area.




## Carry circuit in DPL

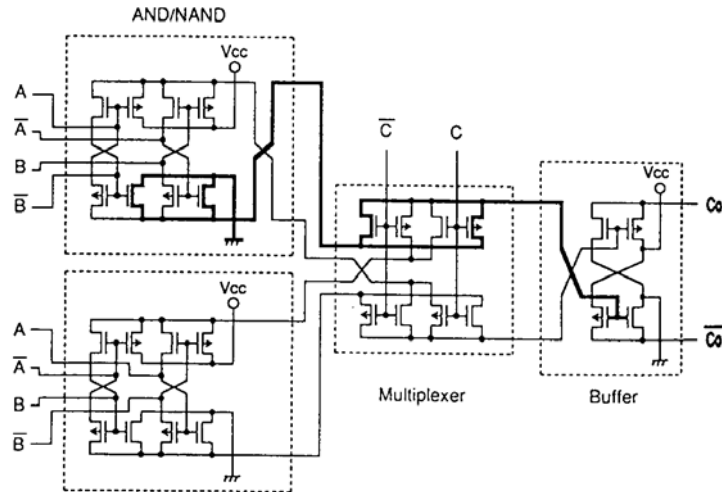

## Power & Speed of DPL

 


## Overall add time of DPL

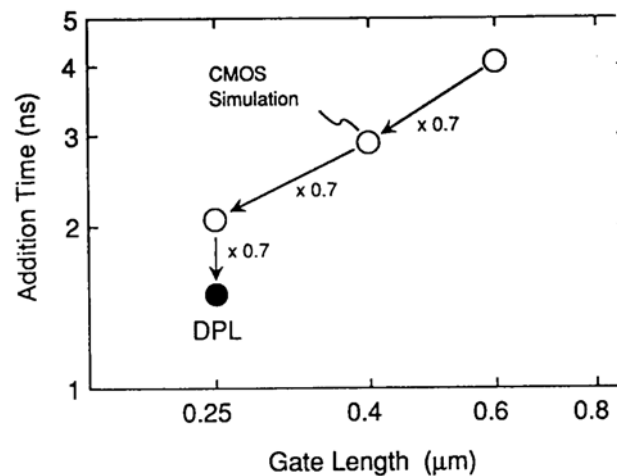
 
## Lean Integration with Pass-Transistor (LEAP)


- ◆ "Top-Down Pass-Transistor Logic Design", K. Yano etc., IEEE J. of Solid-State Circuits, Vol 31, No. 6, June 1996.
- It eliminated the need for keeping a large cell library by replacing a library of 61 basic cells with a new set of THREE library cells called Y1, Y2 and Y3, and 4 inverters of different drive strength.



The gate width of nMOS are  $6\mu\text{m}$ .

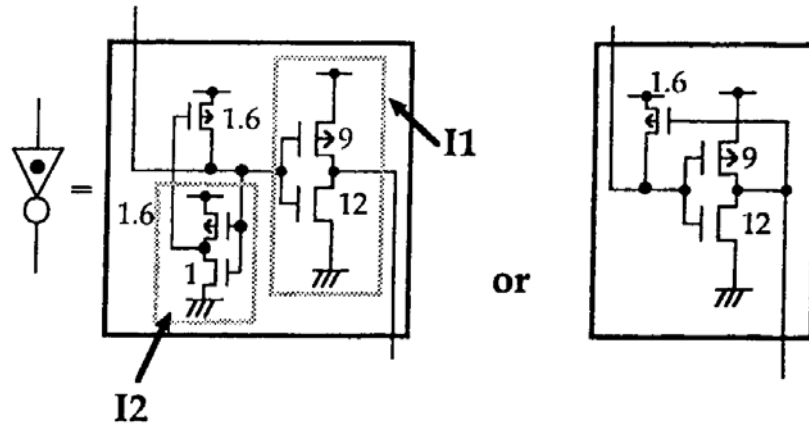
## Inverters used in LEAP

- Note that the inverter on the left is used for driving very large output load and the right inverter for normal load capacitance.


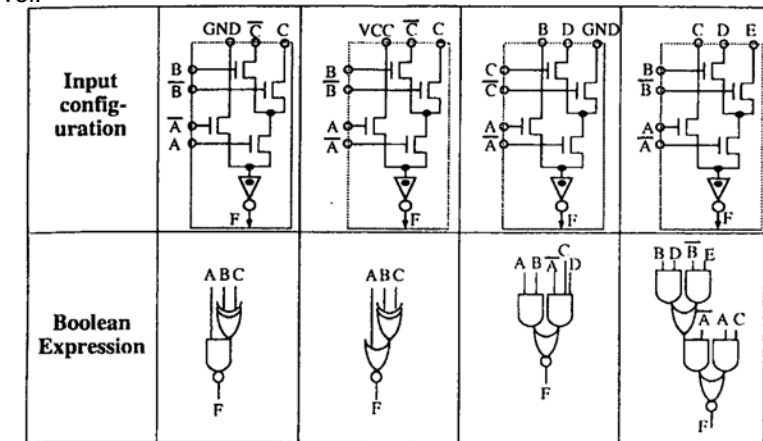
## Y2 can be configured for different logic

- Arbitrary logic circuits can be implemented at almost transistor level, not gate level.



Nov-23-09

E4.20 Digital IC Design


Topic 11 - 17

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 18

## Speed of LEAP

 

## CMOS vs LEAP

	Reported Circuits [18, 19]		Circuit Inventor (This Work)	
	Circuit Diagram		Circuit Diagram	
Full Adder				
Tr. Count	28 (1)		24 (0.86)	
Area	1810 $\mu\text{m}^2$ (1)		1161 $\mu\text{m}^2$ (0.64)	
Delay	0.73 ns (1)		0.32 ns (0.44)	
Power	3.65 $\mu\text{W}/\text{MHz}$ (1)		2.35 $\mu\text{W}/\text{MHz}$ (0.64)	
FOM*	1		6.5	

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 19

Nov-23-09

E4.20 Digital IC Design

Topic 11 - 20